Lecture 9 Digital Filter Structure

Digital Signal Porcessing by Yu Yajun @ SUSTech

473

Block Diagram Representation


 It has advantages to represent time domain inputoutput relation, for example the convolution, or the difference equations, as block diagrams.

$$y[n] = \sum_{k=0}^{N-1} h[k]x[n-k]$$
$$y[n] = \sum_{m=0}^{M} a_m x[n-m] - \sum_{m=1}^{N} b_m y[n-m]$$



A First Order LTI Digital Filter
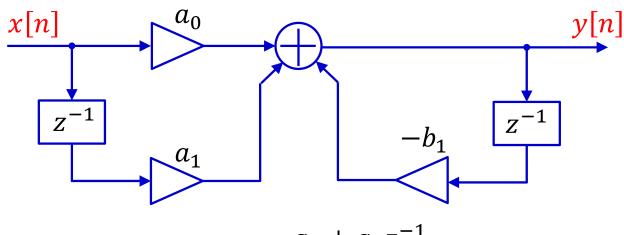
$$y[n] = -b_1y[n-1] + a_0x[n] + a_1x[n-1]$$




$$H(z) = \frac{a_0 + a_1 z^{-1}}{1 + b_1 z^{-1}}$$

Digital Signal Porcessing by Yu Yajun @ SUSTech

475

Analysis of Block Diagrams

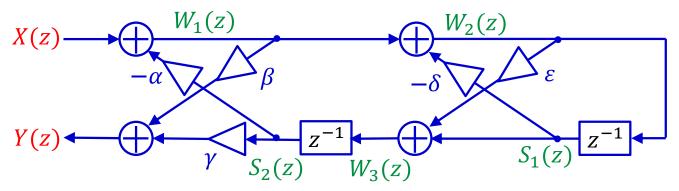

$$W_1 = X - \alpha S_2$$

$$W_2 = W_1 - \delta S_1$$

$$W_3 = \varepsilon W_2 + S_1$$

$$Y = \beta W_1 + \gamma S_2$$

$$S_2 = z^{-1} W_3$$


$$S_1 = z^{-1} W_2$$

$$W_1 = X - \alpha S_2$$
 $S_2 = z^{-1}W_3$ $W_1 = X - \alpha z^{-1}W_3$
 $W_2 = W_1 - \delta S_1$ $S_1 = z^{-1}W_2$ $W_2 = W_1 - \delta z^{-1}W_2$
 $W_3 = \varepsilon W_2 + S_1$ $W_3 = \varepsilon W_2 + z^{-1}W_2$
 $Y = \beta W_1 + \gamma S_2$ $Y = \beta W_1 + \gamma z^{-1}W_3$

$$H(z) = \frac{Y(z)}{X(z)} = \frac{\beta + (\beta \delta + \gamma \varepsilon)z^{-1} + \gamma z^{-2}}{1 + (\delta + \alpha \varepsilon)z^{-1} + \alpha z^{-2}}$$

Delays in Block Diagram

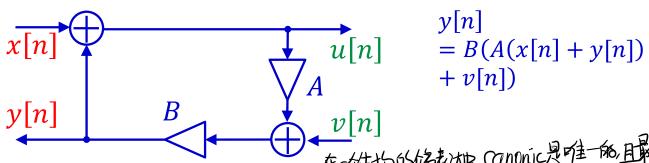• A block diagram containing delay-free loop, i.e., a feedback loop without any delay element, is physically **IMPOSSIBLE** to achieve.



The number of delays in a canonic structure is according to the and a canonic structure is according to the according to the canonic structure is accordi to the order of the transfer function (or the order of the difference equation).


Digital Signal Porcessing by Yu Yajun @ SUSTech

477

Equivalent Structure

$$H(z) = \frac{a_0 + a_1 z^{-1}}{1 + b_1 z^{-1}}$$

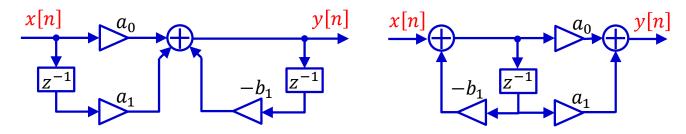Two digital filter structures are defined to be equivalent if they have the same transfer function.



- Transpose Operation to obtain an equivalent structure
 - Reverse all paths
 - Replace branching nodes with adders, and vice versa,
 - Interchange the input and output nodes.

Basic FIR Digital Filter Structures

Direct-Form Structures

$$Y(z) = H(z)X(z) = \sum_{k=0}^{N-1} h[k]z^{-k}X(z)$$

$$y[n] = \sum_{k=0}^{N-1} h[k]x[n-k]$$


$$x[n] \qquad z^{-1} \qquad z^{-1} \qquad z^{-1} \qquad b[3] \qquad h[4] \qquad y[n]$$

$$h[0] \qquad h[1] \qquad h[2] \qquad h[3] \qquad h[4] \qquad y[n]$$

Digital Signal Porcessing by Yu Yajun @ SUSTech

479

Transposed Direct Form Structures

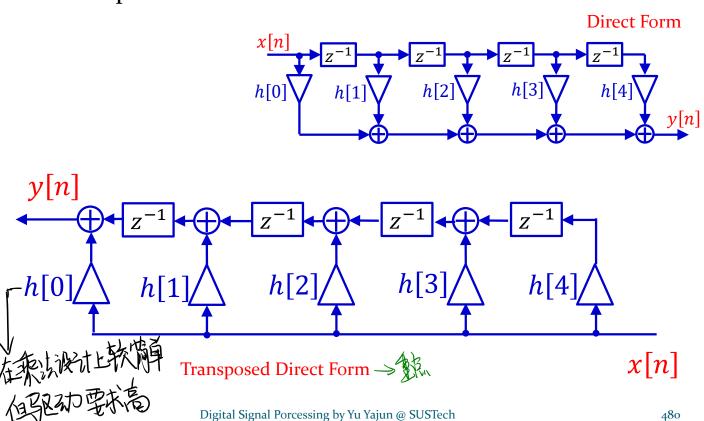


Cascade-Form Structures

$$H(z) = h[0] \prod_{k=1}^{K} (1 + \beta_{1,k} z^{-1} + \beta_{2,k} z^{-2})$$

where K = (N - 1)/2 if N is odd,

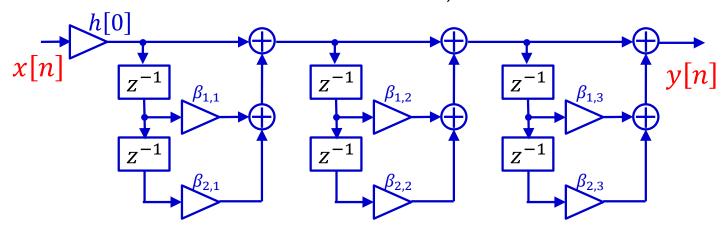and K = N/2 if N is even, with $\beta_{2,K} = 0$



Digital Signal Porcessing by Yu Yajun @ SUSTech

481

impulse response is symmetric.


Linear-Phase FIR Filter Structure

$$h[n] = h[N-1-n]$$
, or $h[n] = -h[N-1-n]$

h[n] = h[N-1-n], or h[n] = -h[N-1-n]• For example, a length-7 Type I filter $\text{Symmetric} \in \text{Nis odd}$

$$H(z) = h[0] + h[1]z^{-1} + h[2]z^{-2} + h[3]z^{-3} + h[2]z^{-4} + h[1]z^{-5} + h[0]z^{-6}$$
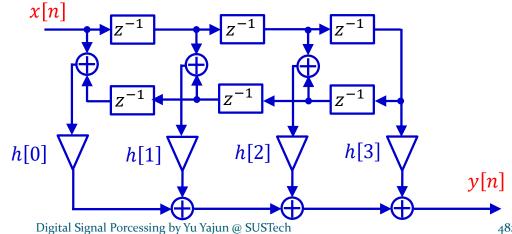
$$= h[0](1+z^{-6}) + h[1](z^{-1}+z^{-5}) + h[2](z^{-2}+z^{-4}) + h[3]z^{-3}$$



482


• a length-8 Type IV filter
$$H(z) = h[0] + h[1]z^{-1} + h[2]z^{-2} + h[3]z^{-1}$$

$$H(z) = h[0] + h[1]z^{-1} + h[2]z^{-2} + h[3]z^{-3}$$

$$-h[3]z^{-4} - h[2]z^{-5} - h[1]z^{-6} - h[0]z^{-7}$$

$$= h[0](1 - z^{-7}) + h[1](z^{-1} - z^{-6})$$
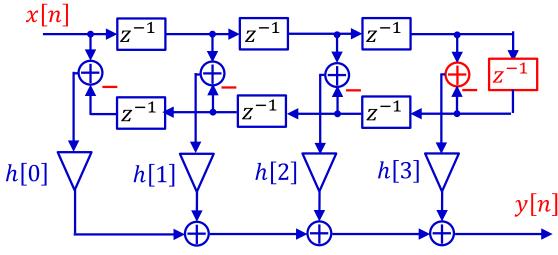
$$+h[2](z^{-2} - z^{-5}) + h[3](z^{-3} - z^{-4})$$



Digital Signal Porcessing by Yu Yajun @ SUSTech

483

Basic IIR Digital Filter Structure

$$y[n] = \sum_{m=0}^{M} a_m x[n-m] - \sum_{m=1}^{N} b_m y[n-m]$$


$$H(z) = \frac{A(z)}{B(z)} = \frac{\sum_{m=0}^{M} a_m z^{-m}}{1 + \sum_{m=1}^{N} b_m z^{-m}} = H_1(z)H_2(z)$$


For example, when M = N = 3, we have


$$H_1(z) = a_0 + a_1 z^{-1} + a_2 z^{-2} + a_3 z^{-3}$$

$$H_2(z) = \frac{1}{1 + b_1 z^{-1} + b_2 z^{-2} + b_3 z^{-3}}$$

Direct-Form Structure

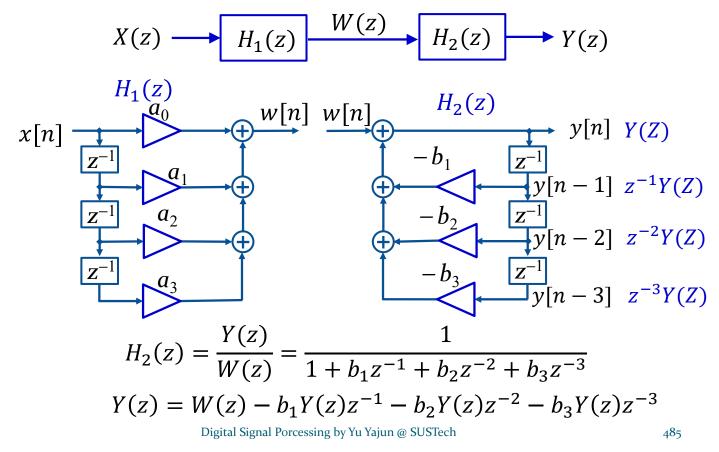

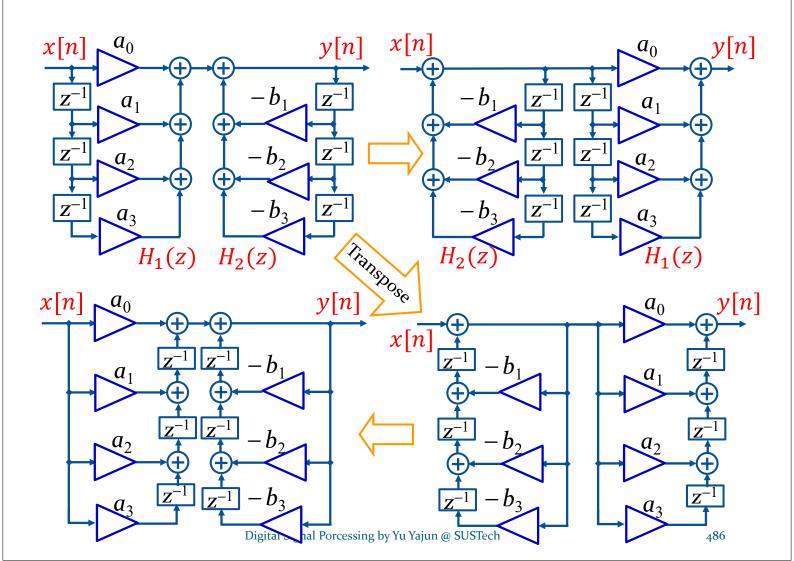

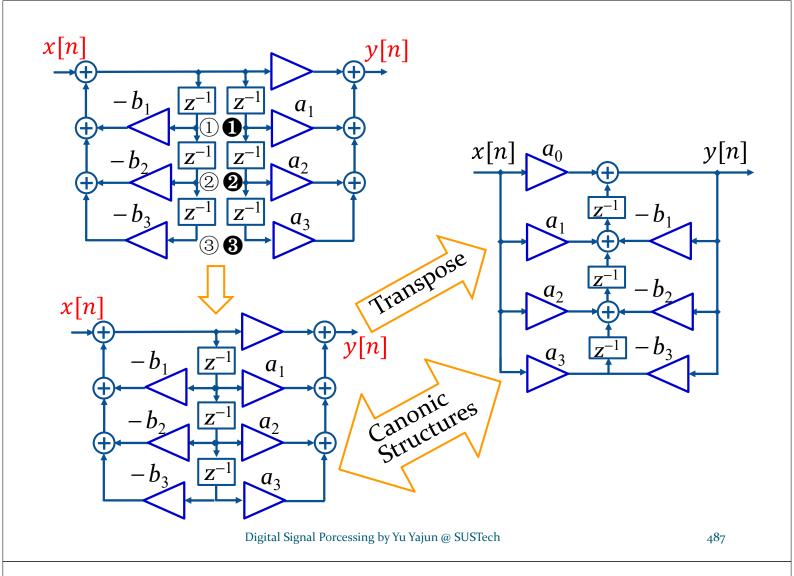

Cascade Realization

$$H(z) = \frac{\prod_{k=1}^{M_1} (1 - f_k z^{-1}) \prod_{k=1}^{M_2} (1 - g_k z^{-1}) (1 - g_k^* z^{-1})}{\prod_{k=1}^{N_1} (1 - c_k z^{-1}) \prod_{k=1}^{N_2} (1 - d_k z^{-1}) (1 - d_k^* z^{-1})}$$

$$H(z) = \frac{B(z)}{A(z)} = \frac{B_1(Z) B_2(Z) B_3(Z)}{A_1(Z) A_2(Z) A_3(Z)}$$


$$+ \frac{B_1(z)}{A_1(z)} + \frac{B_2(z)}{A_2(z)} + \frac{B_3(z)}{A_3(z)} + \frac{B_1(z)}{A_2(z)} + \frac{B_2(z)}{A_3(z)} + \frac{B_3(z)}{A_1(z)} + \frac{B_2(z)}{A_3(z)} + \frac{B_3(z)}{A_2(z)} + \frac{B_3(z)}{A_2(z)} + \frac{B_3(z)}{A_3(z)} + \frac{B_3(z)}{A_3(z)$$

Parallel Realization

$$H(z) = \gamma_0 + \sum_{k} \frac{\gamma_{0k} + \gamma_{1k} z^{-1}}{1 + \alpha_{1k} z^{-1} + \alpha_{2k} z^{-2}}$$


For example:
$$H(z) = \gamma_0 + \frac{B_1(z)}{A_1(z)} + \frac{B_2(z)}{A_2(z)}$$

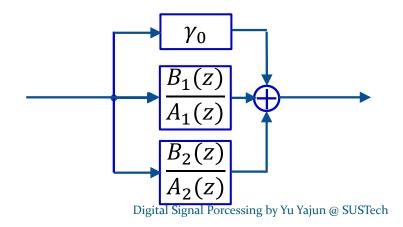Can be obtained by partial-fraction expansion



489


Allpass Filter Structure 等。

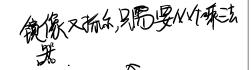

Transfer function of **real** coefficient allpass filter
$$A_{M}(z) = \frac{d_{M} + d_{M-1}z^{-1} + \dots + d_{1}z^{-M+1} + z^{-M}}{1 + d_{1}z^{-1} + \dots + d_{M-1}z^{-M+1} + d_{M}z^{-M}}$$

Objective: efficient structure using N multipliers to implement *N*-th order allpass filter, for example:

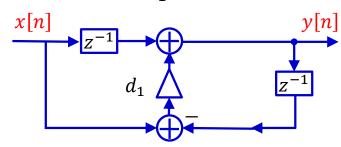
• First order: $A_M(z) = \frac{d_1 + z^{-1}}{1 + d_2 z^{-1}} = \frac{Y(\ge)}{X(z)}$



Digital Signal Porcessing by Yu Yajun @ SUSTech

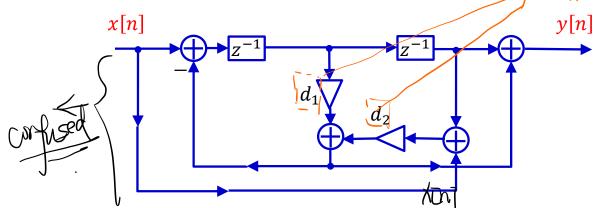• Second order: $A_M(z) = \frac{d_2 + d_1 z^{-1} + z^{-2}}{1 + d_1 z^{-1} + d_2 z^{-2}}$





 Allpass filters with this structure have a magnitude gain of 1 even with coefficient errors

Digital Signal Porcessing by Yu Yajun @ SUSTech

491

晶格

*Allpass with Lattice Structure

- Lattice Stage:
- Suppose G(z) is all pass: $G(z) = \frac{z^{-N}A(z^{-1})}{A(z^{-1})}$

$$V(z) = X(z) - kV(z)G(z)z^{-1}$$

$$V(z) = \frac{1}{1 + kG(z)z^{-1}}X(z)$$

$$Y(z) = kV(z) + V(z)G(z)z^{-1}$$

$$= \frac{k + G(z)z^{-1}}{1 + kG(z)z^{-1}}X(z)$$

$$\frac{Y(z)}{X(z)} = \frac{k + G(z)z^{-1}}{1 + kG(z)z^{-1}} = \frac{kA(z) + z^{-N-1}A(z^{-1})}{A(z) + kz^{-N-1}A(z^{-1})} \triangleq \frac{z^{-(N+1)}D(z^{-1})}{D(z)}$$

$$D(z^{-1} - A(z) + kz^{-N-1}A(z^{-1}) - D(z)$$

Digital Signal Porcessing by Yu Yajun @ SUSTech

G(z)

v[n]

• Obtaining $\{d[n]\}$ from $\{a[n]\}$:

$$d[n] = \begin{cases} 1, \\ a[n] + ka[N - n + 1], \\ k, \end{cases}$$

etaining
$$\{d[n]\}$$
 from $\{a[n]\}$:
$$d[n] = \begin{cases} 1, & n = 0 = 0 \end{cases}$$

$$d[n] = \begin{cases} a[n] + ka[N-n+1], & 1 \leq n \leq N \end{cases}$$
etaining $\{a[n]\}$ from $\{a[n]\}$:
$$d[n] = \begin{cases} a[n] + ka[N-n+1], & 1 \leq n \leq N \end{cases}$$
etaining $\{a[n]\}$ from $\{a[n]\}$:

• Obtaining $\{a[n]\}$ from $\{d[n]\}$:

$$k = d[N+1],$$
 $a[n] = \frac{d[n] - kd[N+1-n]}{1-k^2}$

• If G(z) is stable then $\frac{Y(z)}{X(z)}$ is stable if and only if |k| < 1 $\frac{(k)}{(k)^{N-1}} = \begin{cases} k & \text{if } k < 1 \\ k & \text{if } k < 1 \end{cases}$ The stable then $\frac{Y(z)}{X(z)}$ is stable if and only if |k| < 1.

$$d[N+|-n] = \begin{cases} R, & n = 0 \\ a_{1}(N+|-n] + ka_{1}(N+|-n] + ka_{2}(N+|-n] \\ n = N+|-n| \end{cases}$$


Digital Signal Porcessing by Yu Yajun @ SUSTech

493

494

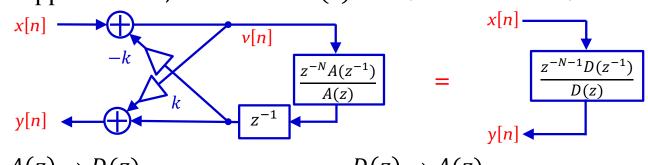Example $A(z) \leftrightarrow D(z)$

Suppose N = 3, k = 0.5 and $A(z) = 1 + 4z^{-1} - 6z^{-2} + 10z^{-3}$



• $A(z) \rightarrow D(z)$

	z^0	z^{-1}	z^{-2}	z^{-3}	z^{-4}
A(z)	1	4	-6	10	
$z^{-4}A(z^{-1})$		10	-6	4	1
D(z)	1	9	-9	12	0.5

$$D(z) = A(z) + kz^{-4}A(z^{-1})$$

D(z)	\rightarrow	\boldsymbol{A}	(z)
ν (ω)		4 1	(~ .

	z^0	z^{-1}	z^{-2}	z^{-3}	z^{-4}
D(z)	1	9	- 9	12	0.5
k = d[N+1]					0.5
$z^{-4}D(z^{-1})$	0.5	12	- 9	9	1
A(z)	1	4	-6	10	

$$A(z^{-1})$$

$$A(z) = \frac{D(z) - kz^{-4}D(z^{-1})}{\text{SUSTech}}$$
Digital Signal Porcessing by Yu Yajun @ SUSTech $1 - k^2$

